

LT3652 MPPT Charger Design Calculations for MicroSun Project

1. Project Overview

This document outlines the design calculations for configuring the LT3652-based MPPT solar battery charger, targeting a 12V SLA battery and a 15W solar panel.

2. Charging Current Sense Resistor (R_SENSE)

Objective: Limit charging current to 1.5A maximum.

Formula:

$$R_SENSE = 0.1 / I_CHG(MAX)$$

Calculation:

$$R_SENSE = 0.1 / 1.5 = 0.0667 \text{ ohms}$$

Recommended: Use standard value **0.068 ohm**, 1% tolerance, $\geq 0.5W$ rated, low TCR.

3. How These Feedback Resistor Values Were Chosen (with LM234)

From the datasheet (Figure 9b), they used this design procedure:

Given:

- TC (temperature coefficient) = $-19.8 \text{ mV}/^{\circ}\text{C}$
- $V_FLOAT (25^{\circ}\text{C}) = 13.8 \text{ V}$
- $R_SET = 2.4 \text{ k}\Omega$ for LM234

Step 1: Compute R_FB1

$$\begin{aligned} R_FB1 &= -R_SET \times (TC \times 4405) \\ &= -2.4\text{k} \times (-0.0198 \times 4405) \\ &= 2.4\text{k} \times 87.219 \approx 209.3 \text{ k}\Omega \end{aligned}$$

Designers approximated this to **210 kΩ** or even **309 kΩ** for tuning.

Step 2: Compute R_FB2

$$R_{FB2} = R_{FB1} / ((V_{FLOAT} + R_{FB1} \times (0.0674 / R_{SET})) / V_{FB} - 1)$$

Where:

- $V_{FB} = 3.3V$ (LT3652 internal reference)
- $V_{FLOAT} = 13.8V$ (target float voltage)
- $R_{SET} = 2.4k\Omega$
- $R_{FB1} = 309k\Omega$

Step 3: Adjust R_FB3 to make $R_{FB2} \parallel R_{FB3} \approx 63.5 k\Omega$ That matches the required divider to bring the VFB node to 3.3 V at the proper V_{FLOAT} .

4. VIN_REG Divider for MPPT (Input Voltage Regulation)

Objective: Hold solar panel input at ~17.6V (V_{mp}) for maximum power point tracking.

Formula:

$$R1/R2 = (V_{IN} / 2.7) - 1$$

Target V_{IN} : 17.6V

Calculation:

$$R1/R2 = (17.6 / 2.7) - 1 \approx 5.52$$

Assume $R2 = 100k\Omega \rightarrow R1 \approx 552k\Omega$

Standard Value Selection:

- $R1 = 549 k\Omega$
- $R2 = 100 k\Omega$

Verification:

$$V_{VIN_REG} = 17.6 * 100 / (549 + 100) \approx 2.71V \quad \checkmark$$

This satisfies the LT3652 requirement to regulate at 2.7V.

5. Summary of Key Design Values

Parameter	Value
Max Charge Current	1.5 A
R_SENSE	0.068 Ω
Feedback Resistors	309k, 174k, 100k
VIN_REG Divider	549k, 100k
